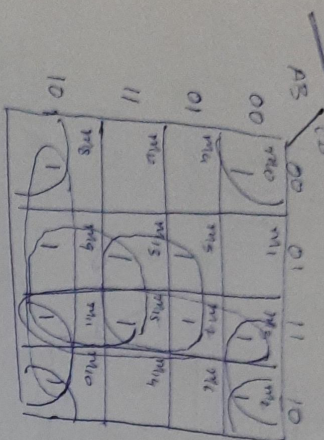


2016

$F(A,B,C,D) = \sum(0,2,3,5,7,8,9,10,13,15)$



One k-map, multiple function.

$$F_1 = BD + B'D' + (s, 9, 10) + (13, 2, 11, 10)$$

$$F_2 = BD + B'D' + (8, 9, 11, 10) + (3, 7, 15, 11)$$

$$F_3 = BD + B'D' + (13, 15, 9, 11) + (3, 2, 11, 10)$$

$$F_4 = BD + B'D' + (13, 15, 9, 11) + (3, 7, 15, 11)$$

Adder:


1 bit half adder:

x_0	y_0	S_0	C_0
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

x_0	y_0	S_0	C_0
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$S_0 = x_0 y_0' + x_0' y_0 = x_0 \oplus y_0$

$C_0 = x_0 y_0$

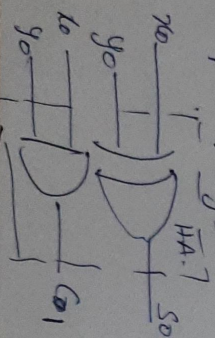

1 bit full adder:

x_i	y_i	S_i	C_i
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1



$S_i = x_i \oplus y_i = C_0 \oplus x_i \oplus y_i$

$C_i = C_1 + S_1 y_1$

$= C_1 + (x_1 \oplus y_1) y_1$

$= C_1 x_1 + (x_1 \oplus y_1) y_1$

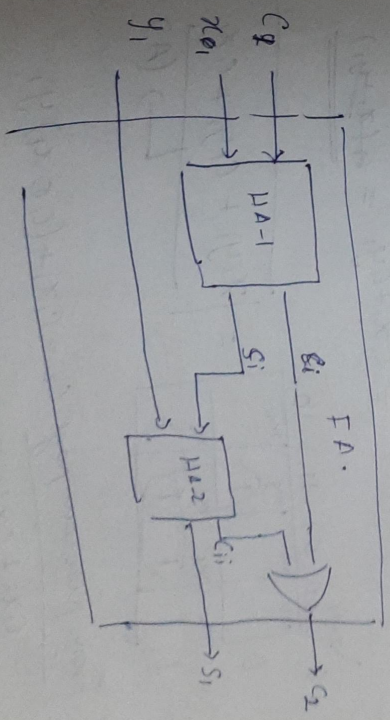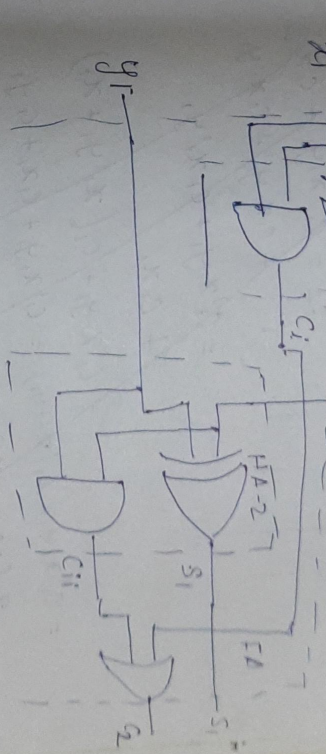Note: $S_i y_i =$ full carry
Carry, call it C_{i+1}
Then $C_i = C_1 + C_{i+1}$



C_q	x_1	y_1	S_1	C_2
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$S_1 = C_1' x_1' y_1 + C_1' x_1 y_1' + C_1 x_1' y_1' + C_1 x_1 y_1$$

$$= C_1' (x_1 \oplus y_1) + C_1 (x_1 \oplus y_1)'$$


$$= C_1' \oplus x_1 \oplus y_1$$

$$C_2 = C_1' x_1' y_1 + C_1 x_1' y_1' + C_1 x_1 y_1' + C_1 x_1 y_1$$

$$= C_1' x_1 y_1 + C_1 x_1' y_1 + C_1 x_1$$

$$\begin{aligned} &= C_1' x_1 y_1 + C_1 (x_1 + y_1) = C_1' x_1 y_1 + C_1 x_1 + C_1 y_1 \\ &= x_1 (C_1' + C_1 y_1) + C_1 y_1 = x_1 (C_1' + y_1) + C_1 y_1 \end{aligned}$$
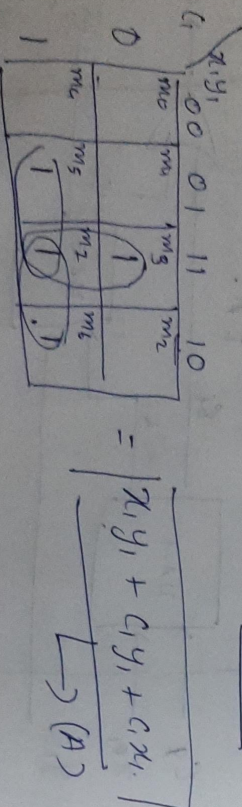
$$= C_1 x_1 + C_1 y_1 = C_1 (x_1 + y_1)$$



From previous page: $C_2 = C_1 x_1 + (C_1 \oplus x_1) y_1$

$$= C_1 x_1 + C_1 x_1' y_1 + C_1' x_1 y_1$$

$$= C_1 (x_1 + x_1' y_1) + C_1' x_1 y_1$$

$$\begin{aligned} &= C_1 x_1 + C_1 y_1 + C_1' x_1 y_1 \\ &= C_1 x_1 + y_1 (C_1 + C_1' x_1) = C_1 x_1 + y_1 (C_1 + x_1) \\ &= C_1 x_1 + C_1 y_1 + x_1 y_1 \rightarrow (B) \end{aligned}$$

$$(A) = (B) \quad \therefore$$

23-8-16 Look ahead carry generator:

Depends 2 variables $P_i = A_i \oplus B_i$, $G_i = A_i B_i$

$C_{i+1} = G_i + P_i C_i$ (Note this is same as the expression $G_4 = C + S_1 S_2 (y_1)$ derived before)

G_i = carry generator.

P_i = carry propagator (propagates carry from previous stage).

$$P_0 = A_0 \oplus B_0 \rightarrow (1), G_0 = A_0 B_0 \rightarrow (2)$$

$$C_1 = G_0 + P_0 C_0 \rightarrow (3)$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 (G_0 + P_0 C_0) = G_1 + P_1 G_0 + P_1 P_0 C_0 \rightarrow (4)$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0)$$

$$= G_2 + P_2 (G_1 + P_1 (G_0 + P_0 C_0)) = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0 \rightarrow (5)$$

$$C_4 = G_3 + P_3 C_3 = G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0))$$

$$= G_3 + P_3 (G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0)) = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0 \rightarrow (6)$$