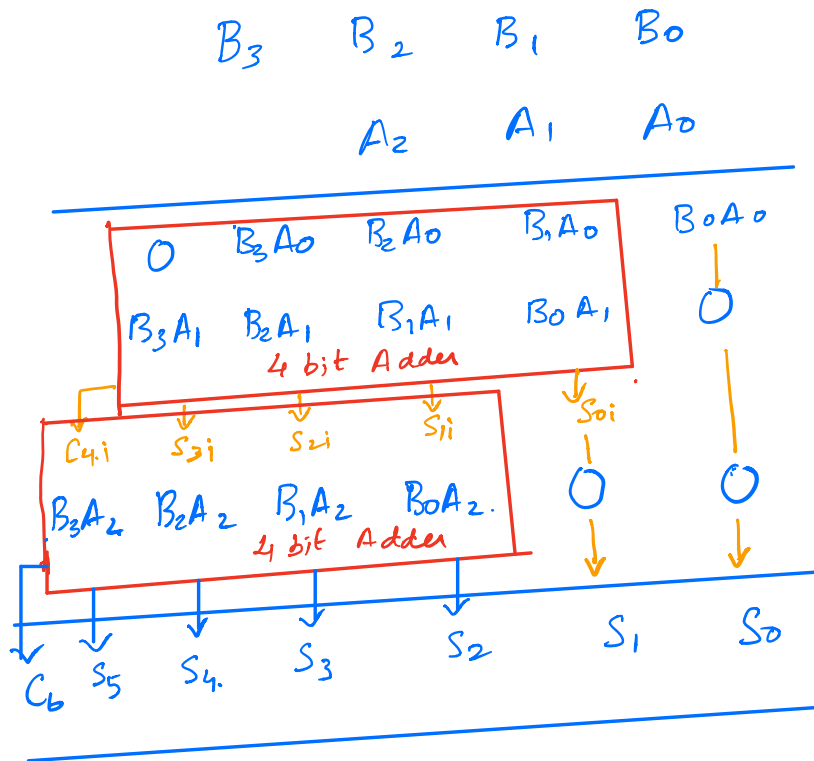


4 bit X 3 bit Multiplier




Decoder Applications:

m input lines

2^m output lines. The m input lines can be considered as addresses that access say 2^m peripheral devices.

For example:

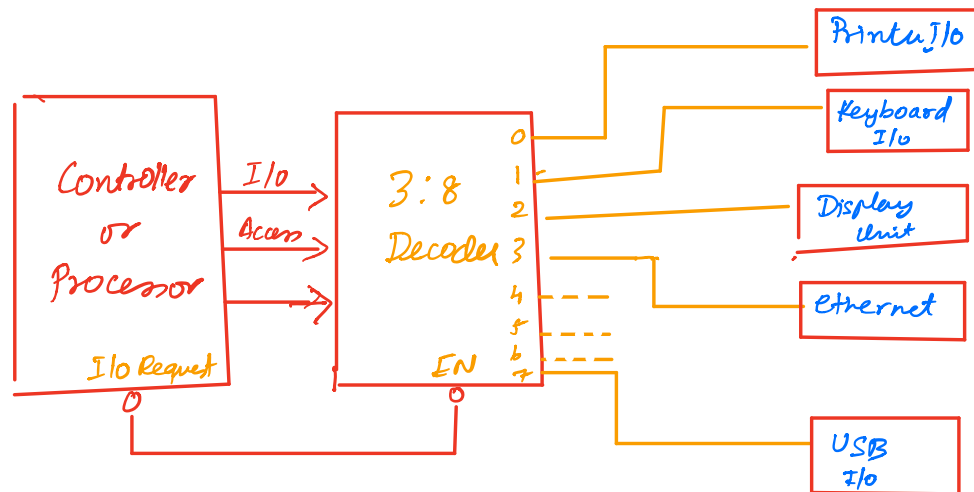

Keyboard Encoder:

