
Again D-Type Edge Triggered FF:

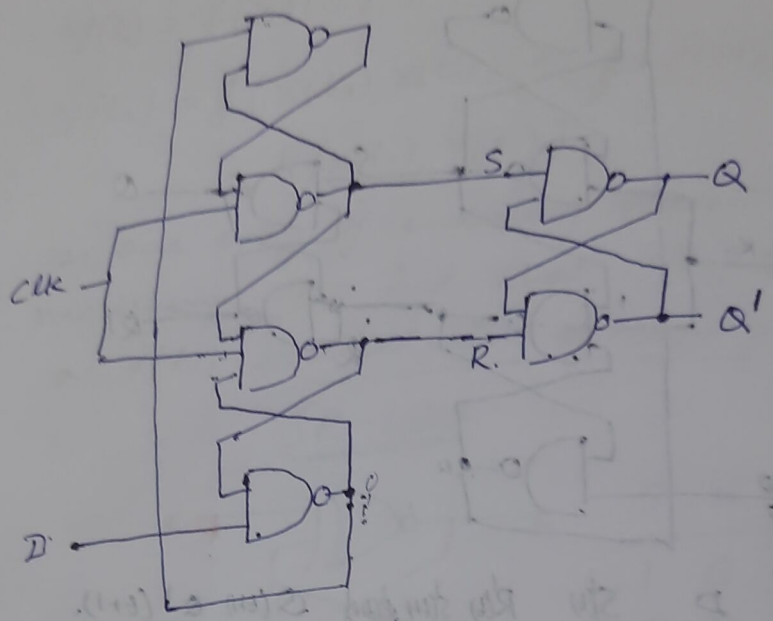

D Clk	D	S(t)	R(t)	S(t+1)	R(t+1)	Q(t+1)	Q'(t+1)
⊓	X	X	X	1	1	Q(t)	Q'(t)
⊓	0	1	1	1	0	0	1
⊓	1	1	0	1	0	0	1
Change in D after ↑ has no effect on S(t+1), R(t+1) and hence Q(t+1)							
⊓	1	1	0	1	1	0	1
⊓	1	1	1	0	1	1	0
→ Though D changed state immediately after rising edge has to wait until next rising edge for Q to change.							
⊓	0	0	1	0	1	1	0
Subsequent change to D after rising edge has no effect on Q(t+1).							